

I can make predictions and record my findings in a table.

## Working Circuits?

Fill in the table giving a reason for your prediction, and then use a tick or a cross to indicate whether or not it is a working circuit

<b>Circuit</b>	<b>Prediction</b>	<b>Result</b>
<b>1</b>	I think the light will/will not light because .....	
<b>2</b>		
<b>3</b>		
<b>4</b>		
<b>5</b>		
<b>6</b>		
<b>7</b>		
<b>8</b>		
<b>9</b>		
<b>10</b>		